
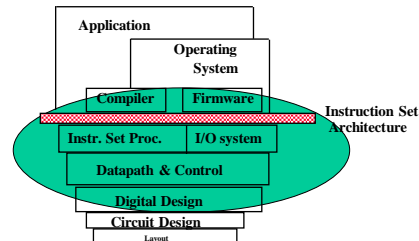


CS/SE 3340

Computer Architecture

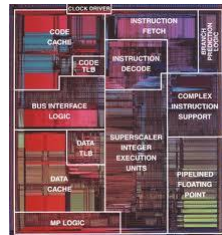


Building the Processor – Data Path & Control

Adapted from slides by Profs. D. Patterson and J. Hennessey

Questions

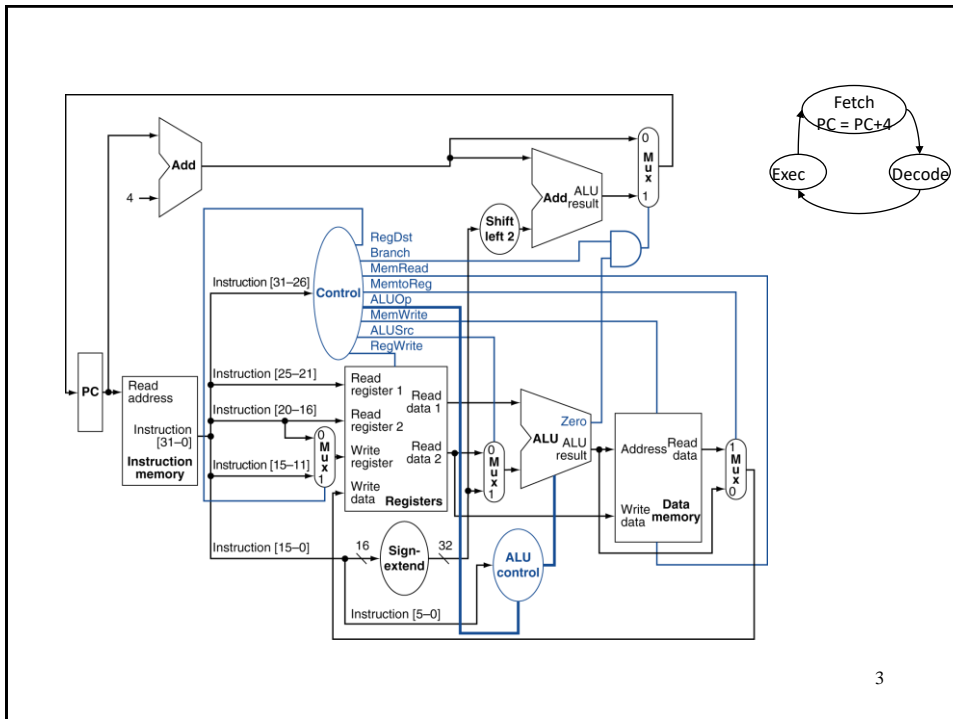
1. How instructions are executed by a processor?
2. What/Why of **control** and **datapath**
3. How data/info is processed by the datapath for *arithmetic/load and store/branching* type instructions?
4. How the ALU is **controlled**?
5. What are the basics of logic design?



3


Instruction Execution

 - PC → instruction memory, fetch instruction
 - PC is automatically updated to PC + 4 (*why?*)
- Register numbers → register file, read/write registers
- Depending on instruction type
 - Use the **ALU** to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC ← target address or PC + 4: *next instruction*



4


CPU Overview

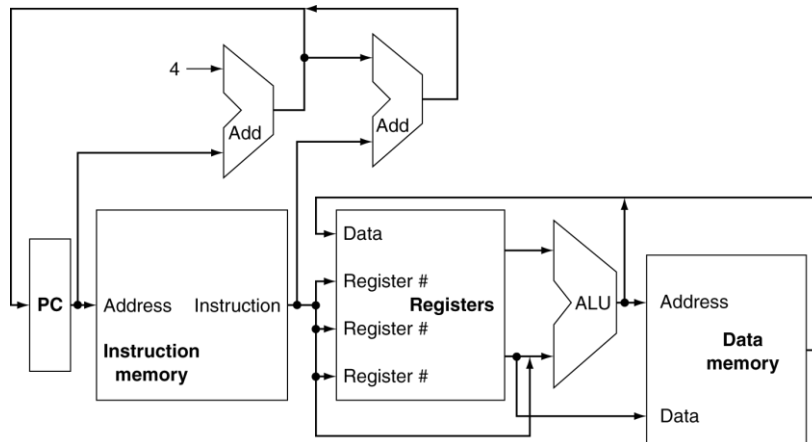

- Can't just join wires together
- Must use *multiplexers*


5

Multiplexers

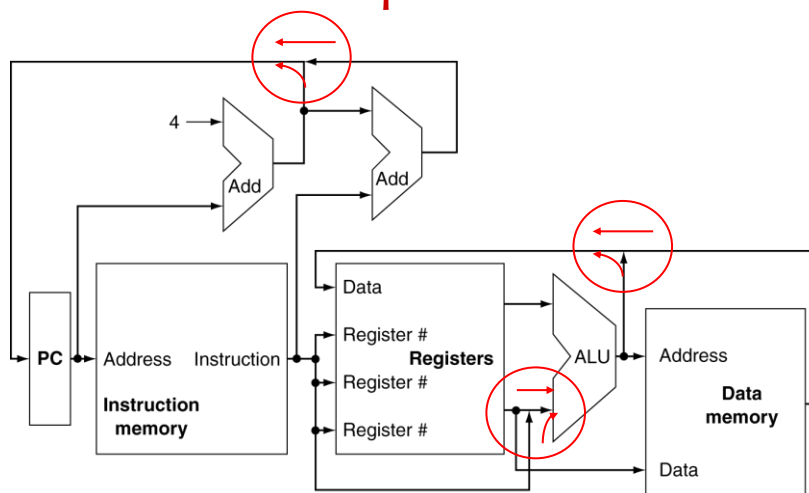

6

Control

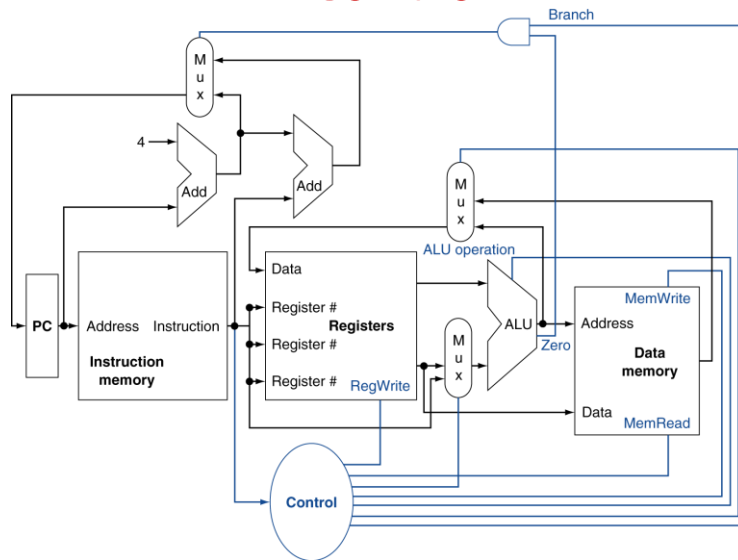


7

Building a Datapath

- Datapath
 - Elements that process data and **addresses** in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design

8


Instruction Fetch

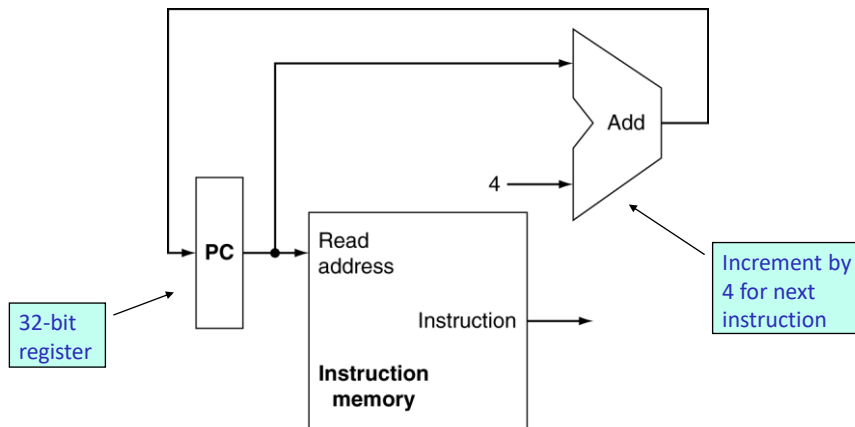

9

Arithmetic/Logical Instructions

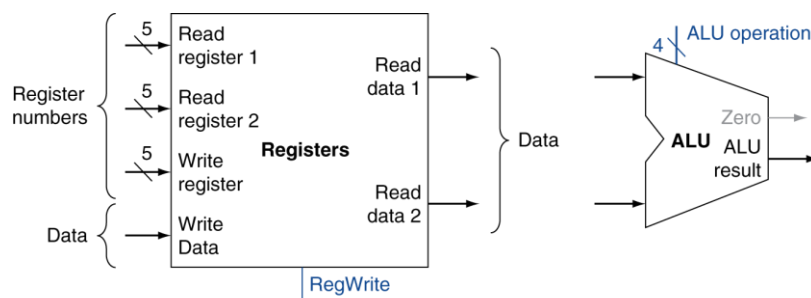- Read two register operands
- Perform arithmetic/logical operation
- Write register result




a. Registers

b. ALU

10

Load/Store Instructions

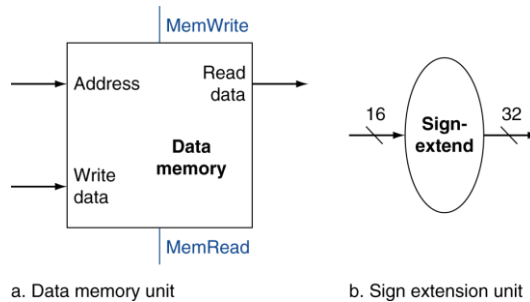- Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




11

Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch

12

Branch Instructions

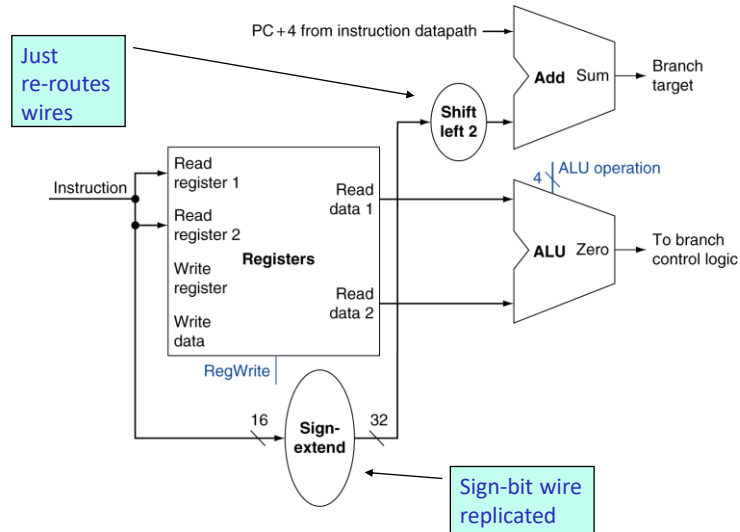


13

Composing the Elements

- First-cut data path does an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions


14

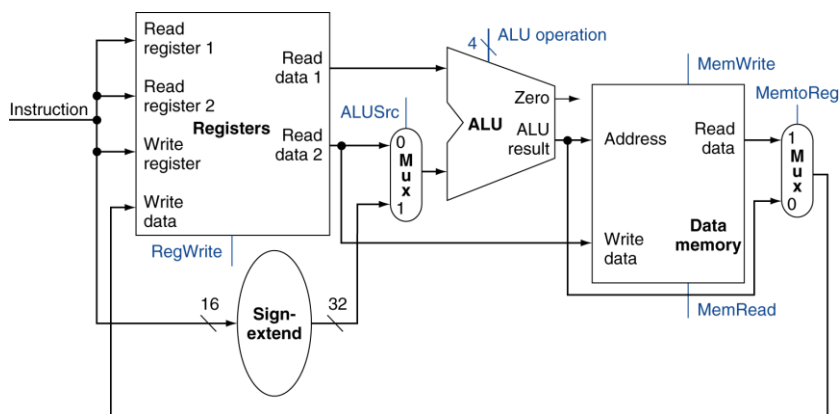Arithmetic or Logical/Load/Store Datapath



15

Full Datapath

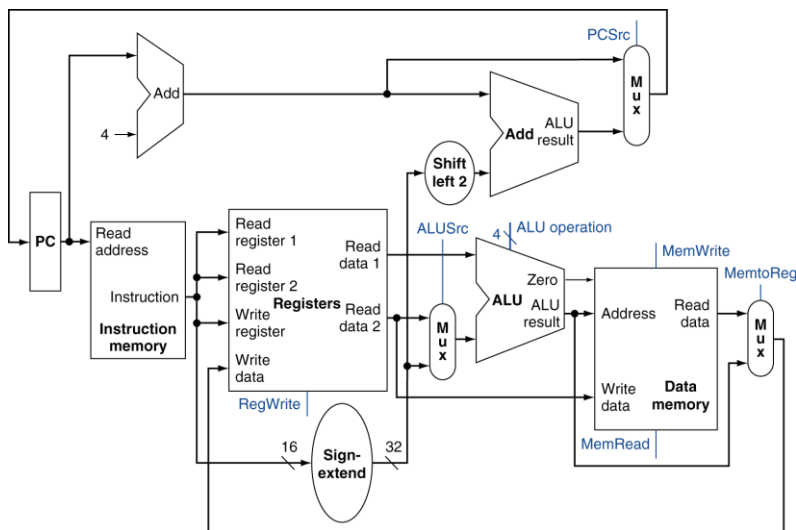

16

ALU Control

- ALU is used for
 - Load/Store: F = add
 - Branch: F = subtract
 - R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

17

ALU Control


- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

18


The Main Control Unit

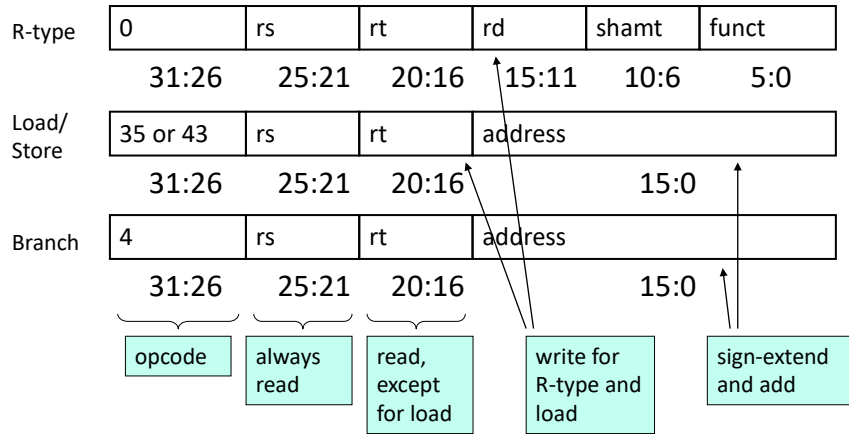- Control signals derived from instruction




19

Datapath With Control

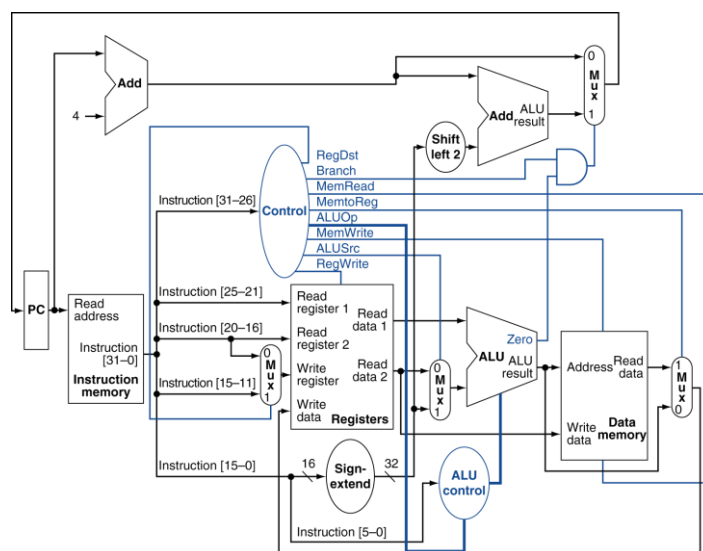


20

R-Type Instruction

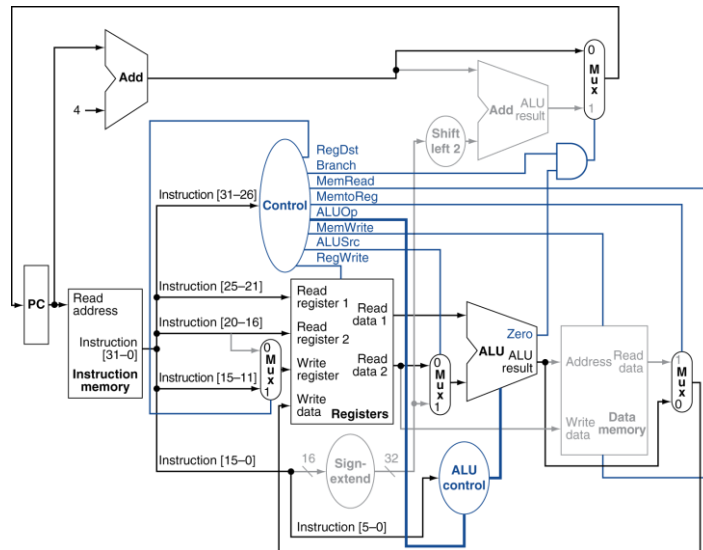


21

Load Instruction

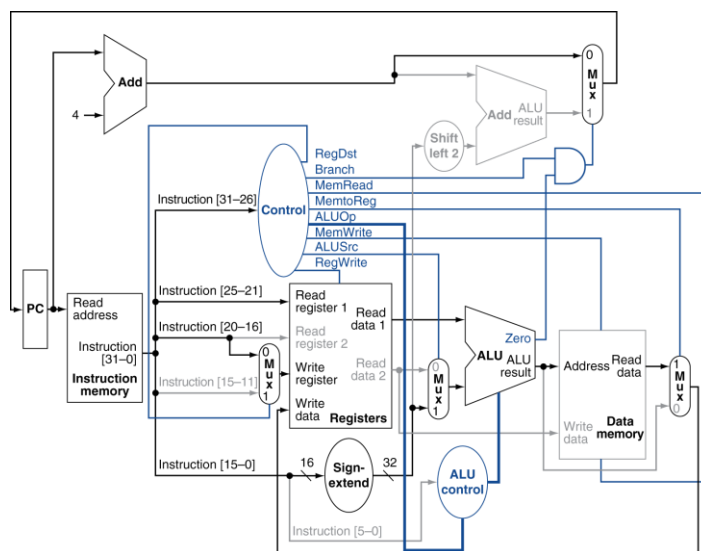

22

Branch-on-Equal Instruction

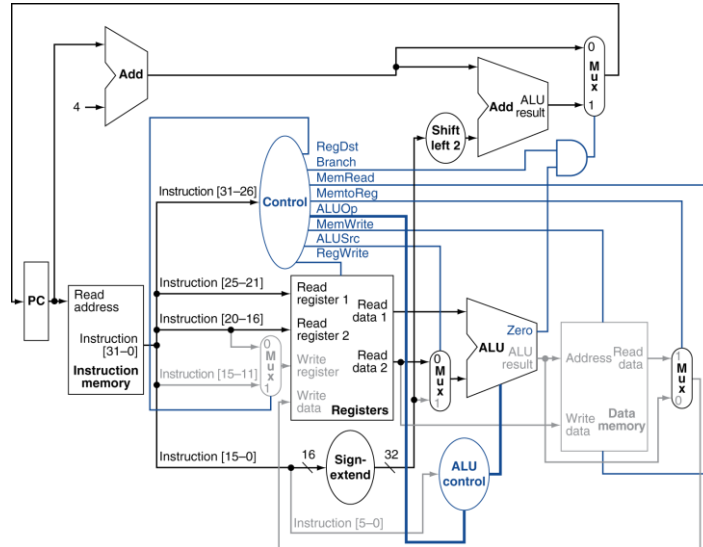


Implementing Jumps

Jump	2	address
	31:26	25:0

- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of old PC
 - 26-bit jump address
 - 00
- Need an extra control signal decoded from opcode

24

Datapath With Jumps Added

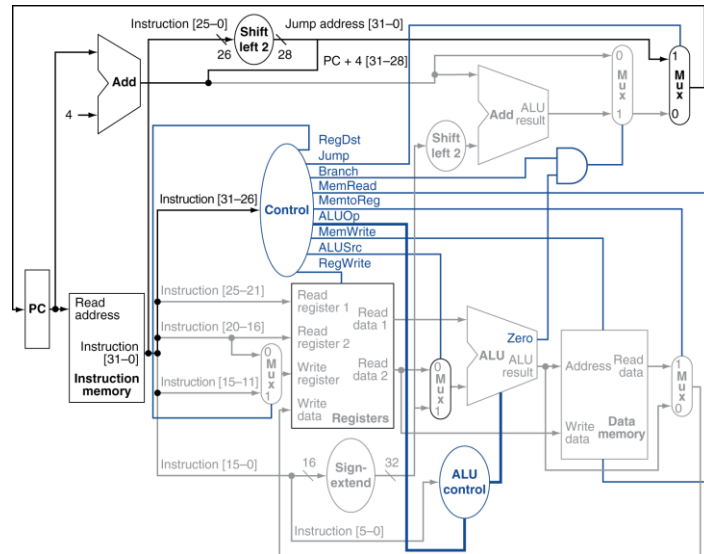

Logic Design Basics


- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational elements
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information, behavior depends on state

26

Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Adder

- $Y = A + B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 

- Arithmetic/Logic Unit

- $Y = F(A, B)$


 


27

Sequential Elements

- Register: stores data in a circuit

  
- Uses a *clock signal* to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1



28


Sequential Elements

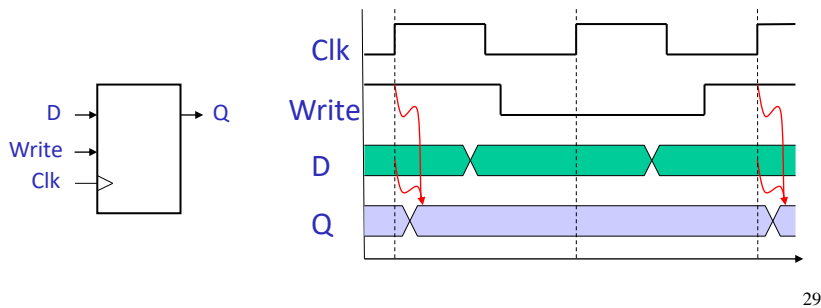- Register with write control
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Clocking Methodology

 - Combinational logic transforms data during clock cycles
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period



Summary

- To build a processor we need to build a ***data path*** and a ***control*** unit
- Multiplexers are needed to select (“merge”) inputs
- A data path and control for a simple (single cycle) processor that supports most instruction types were examined
- At hardware (circuit) level **combinational** and **sequential** logics are needed for this purpose

31